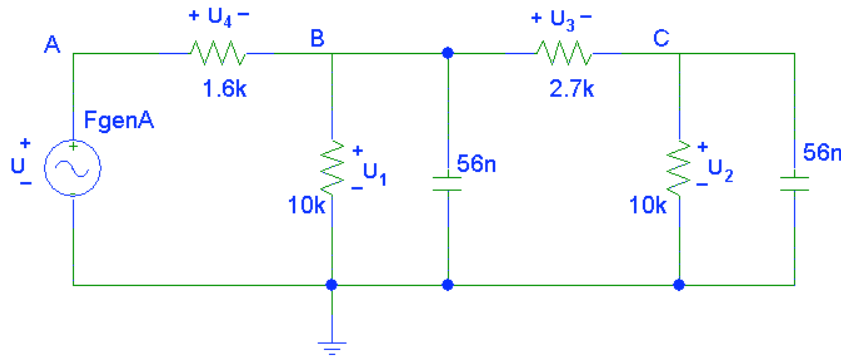


**SHORT INSTRUCTION MANUAL FOR GUEST EXPERIMENTS**

**1 Kirchoff's voltage law**

The circuit in the Figure is used to check Kirchoff's voltage law. Wire the circuit and set the function generator to 5 Vpp and 1000 Hz. If you are unable to read the color code or numerical value of a component the nominal value will be displayed to the lower right of the breadboard when you point at the component.



Measure the voltages  $U_1$ ,  $U_2$  and  $U_3$  with a multi-meter and fill in the table.

$U_1$	$U_2$	$U_3$	$U_1 - U_3 - U_2$

Calculate  $U_1 - U_3 - U_2$  and fill in the value in the table above.


The result is not zero, but according to KVL it should be zero or ...

The reason for the non zero result is that the multi-meter does not take into consideration the relative phase between the various voltages, but instead only shows the effective AC values.

Exchange the DMM for the oscilloscope and measure  $U$ ,  $U_1$  and  $U_2$ . Use the phase of  $U$  as a reference phase and fill in the complex values for the various voltages in the table.

	$U$	$U_1$	$U_2$
Amplitude (Vrms)			
Phase °			

 Draw a scale diagram showing the voltages  $U$ ,  $U_1$  and  $U_2$ .



Highlight and measure the voltages  $U_3$  and  $U_4$  in the diagram.  
 Also measure the voltages  $U_3$  and  $U_4$  with a multi-meter. Fill in the table.

Measured in diagram		Measured with multi-meter	
$U_3$	$U_4$	$U_3$	$U_4$

## 2 Operational amplifier

The data sheet for the uA741 operational amplifier can be downloaded from <http://www.datasheetcatalog.org/datasheet/texasinstruments/ua741.pdf>. You can, for example, wire the following circuit and measure the slew rate with the oscilloscope or exchange R1 for the DMM and measure the short-circuit output current with the DMM.

